



UNIVERSITY OF TEHRAN
Electrical and Computer Engineering Department
Digital Logic Design, ECE 367 / Digital Systems I, ECE 894
Fall 1402
Homework 4
Karnaugh-Map, Hazards

Name:	Date:
Username:	

1. Using Boolean algebra rules minimize the following function and show the NAND realization of the minimized functions.

$$f(a,b,c,d) = a'.b'.c.d' + a'.b.c' + b.c.d + a'.c.d' + b'.c.d' + a.b'.c$$

2. Using Boolean algebra rules minimize the following function and show the NOR realization of the minimized functions.

$$f(a,b,c,d) = a'.b'.c' + a'.b'.c + a.b' + b'.c'.d + b'.c.d'$$

3. Minimize the following function using NOT, 2-input and 3-input NAND gates. the delays of these gates are #6, #5, and #8 NS respectively.
- Show all NAND implementation of this circuit resulted from the two-level minimized circuit. Find the worst-case delay value.
 - Show NAND implementation using only gates listed above. Find the worst-case delay value.
 - Arrange the gate structure of Part b in such a way to reduce the worst-case delay of the circuit, still using only gates listed above. Find the worst-case delay value.
 - Write SystemVerilog description of Part c using SystemVerilog primitives.
 - Using the worst-case delay of Part c, write SystemVerilog description of this circuit using an **assign** statement.
 - Find input transitions that the circuit of Part a and Part c have different timing behaviors.

$$f(a,b,c,d) = \sum_m (3, 4, 5, 10, 11, 13, 14, 15)$$

4. For the given circuit,
- List all potential static hazards
 - List the logical hazards including their duration, the time they occur and input transition causing them
 - Of all logical hazards, list those that are also considered as electrical hazards, and
 - If the output gate drives two gates similar to its own input, then which of the logical hazards also become electrical hazard?

$$f(a,b,c,d) = \sum_m (1, 3, 4, 5, 10, 11, 14, 15)$$

5. Show all minimal two-level SOP minimizations for the following function. Show the circuit using 2-input NAND gates only.

$$f(a,b,c,d) = \sum_m (0, 1, 3, 4, 5, 10, 11, 12, 14), d(13, 15)$$

6. Show all minimal two-level POS minimizations for the following function. Show the circuit using 2-input NOR gates only.

$$f(a,b,c,d) = \sum_m (0, 1, 3, 4, 5, 10, 11, 12, 14), d(13, 15)$$

7. Use tabular QM minimization method to reach the minimal realization of the function shown below. Show all necessary steps and tables.

$$f(a,b,c,d) = \sum_m (0, 1, 3, 4, 5, 10, 11, 12, 14), d(13, 15)$$

8. Show all forms of two-level POS minimizations for the following function.

$$f(a,b,c,d) = \prod_M (0, 1, 3, 4, 5, 10, 11, 12, 14), d(13, 15)$$

9. Show all forms of two-level SOP minimizations for the following function.

$$f(a,b,c,d) = \prod_M (0, 1, 3, 4, 5, 10, 11, 12, 14), d(13, 15)$$